
Block diagram

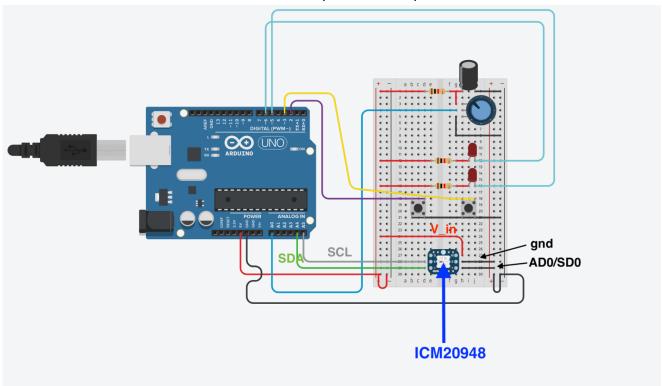The shield should be able to accommodate the requirements as pictured:




- 1. Two LEDs (Spec) with appropriate resistors (Spec) connected to PORTD pins 5&6 in reverse logic.
- 2. Two push buttons (spec) working in internal pullup mode connected to PORTD pins 2&3.
- 3. A 10K Potentiometer (spec) with a filter connected to PORTC pin 0.
- 4. Female header pin for I2C interface with VCC and GND to accommodate the ICM20948 sensor (link to lib will be updated).

Connection Summary:

- PC4-PC5: I2C,
- PC0: POT,
- PD2,PD3: Switch
- PD6, PD5: Led

The capacitor is not specified.

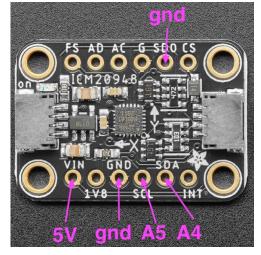


Using the ICM20948 AdaFruit module, the spacing can be built correctly. This module requires 5 pins to operate in I2C mode.

Potentiometer


https://www.digikey.com/en/products/detail/bourns-inc/3362P-1-

103LF/1088412?utm_adgroup=Trimmer%20Potentiometers&utm_source=google&utm_medium=cpc&utm_campaign=Shopping_Potentiometers%2C%20Variable%20Resistors_NEW&utm_term=&utm_content_t=Trimmer%20Potentiometers&gclid=EAIaIQobChMI1MzYvODt6AIVIK_sCh3QgAILEAYYAyABEgL7wvD_B

wE

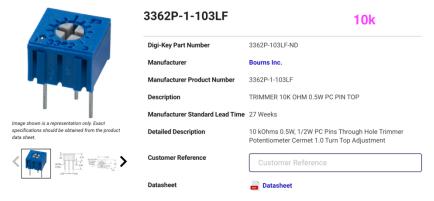


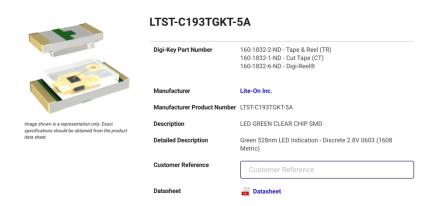LEDs, x2 https://www.digikey.com/en/products/detail/lite-on-inc/LTST-C193TGKT-5A/2356255




Push button, x2

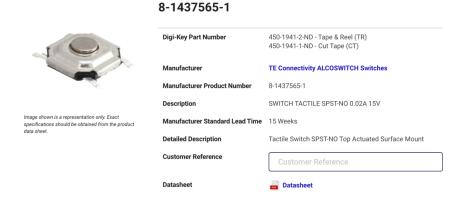https://www.digikey.com/en/products/detail/te-connectivity-alcoswitch-switches/8-1437565-1/529677




Resistor, x3

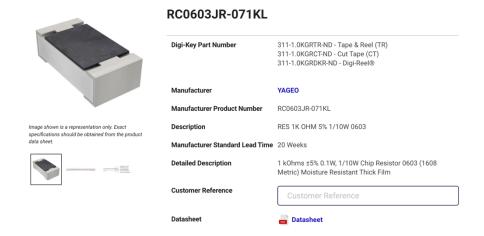https://www.digikey.com/en/products/detail/yageo/RC0603JR-071KL/726677




Capacitor

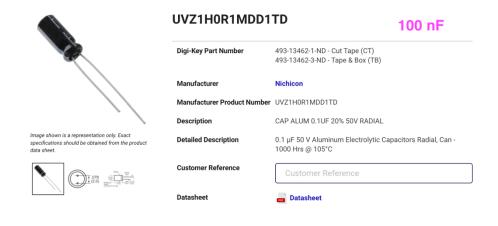https://www.digikey.com/en/products/detail/nichicon/UVZ1H0R1MDD1TD/4342173




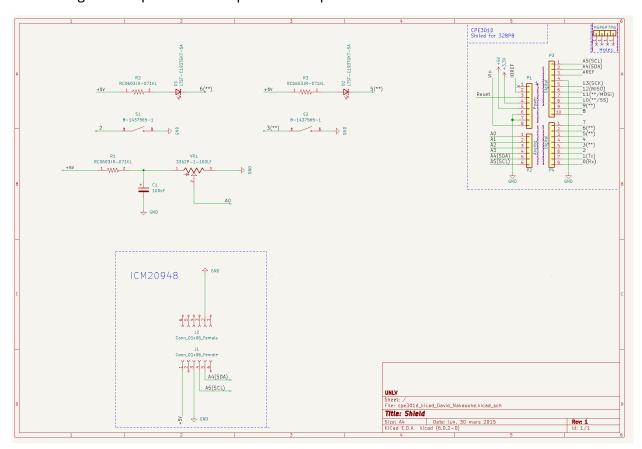New project, from template, using the Arduino Uno. Downloading the footprints for the specified components:




The netlist and BOM were also made


Performing the DRC:

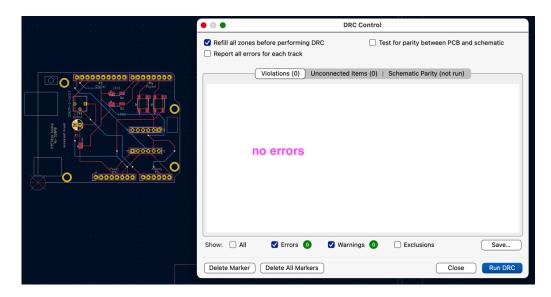


The shield, using 2 layers:

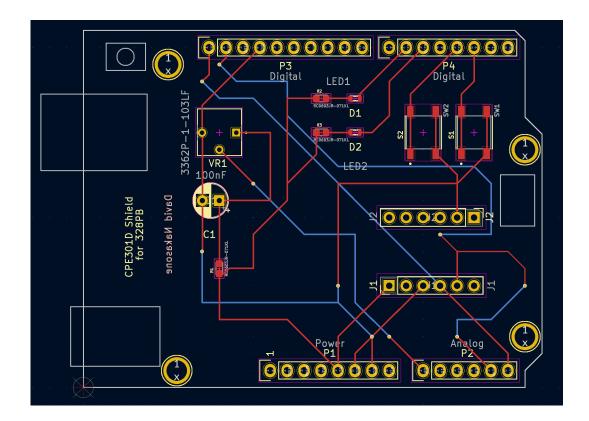

Back of shield:

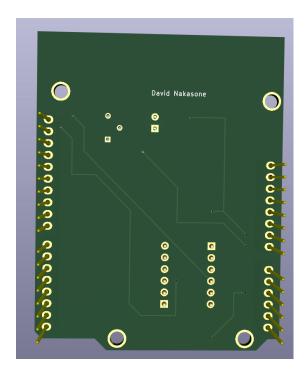


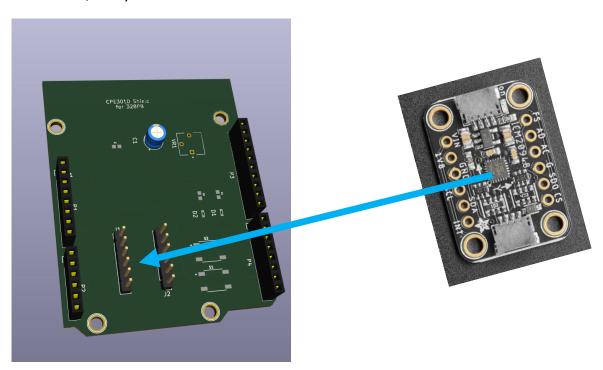Front of shield, ready for the ICM20948 to be soldered on:



I was unwilling to pay for the 3D footprint models.

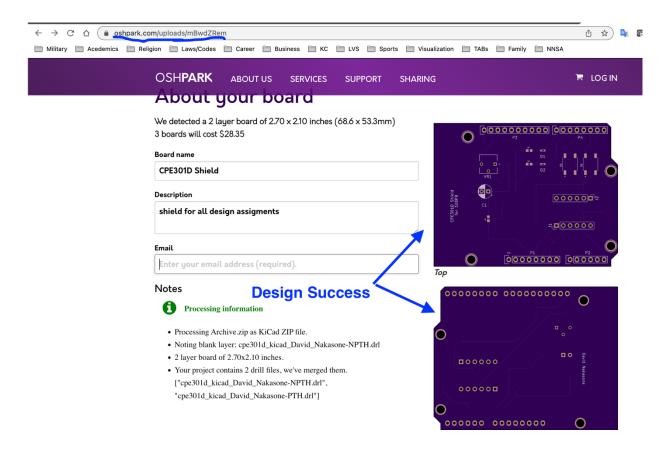Outputting the design files (Gerber and Drill), the design is successful:



See the github:

https://github.com/davenakasone/cpe301 David Nakasone/tree/main/kicad